

Name: _____

Key

Practice - 21.1 Resistors in Series and Parallel

1. You have ten 275- Ω resistors.

A. What is the resistance of these resistors if they are connected in series?

$$R_{\text{eq}} = R_1 + R_2 + \dots + R_{10} = 10(275\Omega) = \boxed{2750\Omega}$$

B. A. What is the resistance of these resistors if they are connected in parallel?

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_{10}} = \frac{10}{275\Omega} \Rightarrow R_{\text{eq}} = \boxed{27.5\Omega}$$

2. You have a 1.00×10^2 - Ω resistor, a 2.50-k Ω resistor and a 4.00-k Ω resistor.

A. What is the resistance of these resistors if they are connected in series?

$$R_{\text{eq}} = \sum_i R_i \Rightarrow R_{\text{eq}} = 1.00 \times 10^2 + 2.50 \times 10^3 + 4.00 \times 10^3 \Omega = \boxed{6.60 \times 10^3 \Omega} = 6.60 \text{ k}\Omega$$

B. A. What is the resistance of these resistors if they are connected in parallel?

$$\frac{1}{R_{\text{eq}}} = \sum_i \frac{1}{R_i} \Rightarrow R_{\text{eq}} = \frac{1}{0.100 \text{ k}\Omega} + \frac{1}{2.50 \text{ k}\Omega} + \frac{1}{4.00 \text{ k}\Omega} \Rightarrow R_{\text{eq}} = \boxed{93.9\Omega}$$

3. What are the largest and smallest resistances you can obtain by connecting a 36.0- Ω , a 50.0- Ω and a 700- Ω resistor together?

$$R_{\text{largest}} = R_{\text{series}} = 36.0 + 50.0 + 700 = \boxed{786\Omega}$$

$$R_{\text{smallest}} = R_{\text{parallel}} \Rightarrow \frac{1}{R_{\text{eq}}} = \frac{1}{36} + \frac{1}{50} + \frac{1}{700} \Rightarrow R_{\text{eq}} = \boxed{20.3\Omega}$$

4. An 1800-W toaster, a 1400-W electric frying pan, and a 75-W lamp are plugged into the same outlet in a 15-A, 120-V circuit. (Note: The three devices are in parallel when plugged into the same socket.)

A. What current is drawn by each device?

$$P = IV \Rightarrow I = \frac{P}{V}$$

$$I_{\text{toaster}} = \frac{1800\text{W}}{120\text{V}} = \boxed{15.0\text{A}}$$

$$I_{\text{lamp}} = \frac{75\text{W}}{120\text{V}} = \boxed{0.63\text{A}}$$

$$I_{\text{fry pan}} = \frac{1400}{120\text{V}} = \boxed{11.7\text{A}}$$

B. Will this combination blow the 15-A fuse?

$$I_{\text{toaster}} + I_{\text{fry pan}} = 26.7\text{A} > 15\text{A} \quad \boxed{\text{Yes}}$$

5. You have a 48.0-V battery and 24.0- Ω and 96.0- Ω resistors.

A. Find the current and power for each resistor when connected in series.

$$I = \frac{V}{R} = \frac{48.0\text{V}}{24.0 + 96.0\Omega} = \boxed{0.400\text{A}} = I_{24\Omega} = I_{96\Omega}$$

$$P_{24\Omega} = I^2 R = (0.400\text{A})^2 (24.0\Omega) = \boxed{3.84\text{W}} \quad P_{96\Omega} = (0.400\text{A})^2 (96.0\Omega) = \boxed{15.4\text{W}}$$

B. Find the current and power for each resistor when connected in parallel.

$$I_{24\Omega} = \frac{V}{R} = \frac{48.0\text{V}}{24.0\Omega} = \boxed{2.00\text{A}} \quad I_{96\Omega} = \frac{48.0\text{V}}{96.0\Omega} = \boxed{0.500\text{A}}$$

$$P_{24\Omega} = IV = (2.0\text{A})(48.0\text{V}) = \boxed{96.0\text{W}} \quad P_{96\Omega} = (0.500\text{A})(48.0\text{V}) = \boxed{24.0\text{W}}$$