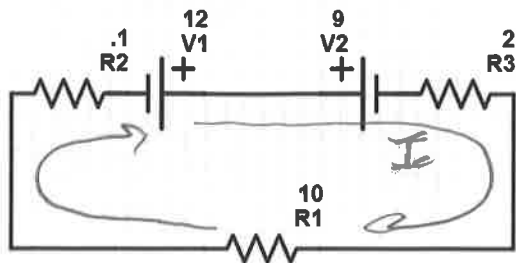



Kirchoff's Laws #1



Loop Rule: $12V - 9V - 2I - 10I - 0.1I = 0$

$3V = 12.1I$

$I = \frac{3V}{12.1\Omega} = 0.248A$

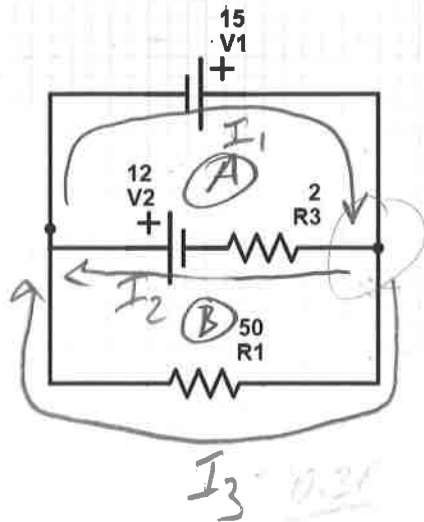

Junction Rule!

$$I_1 = I_2 + I_3$$

Loop A: $15V - 2I_2 + 12V = 0$
 Clockwise

$$I_2 = \frac{27}{2} A = 13.5 A$$


Loop B:
 (CCWise)

$$12V + 50I_3 - 2I_2 = 0$$

$$50I_3 = 15V$$

$$I_3 = \frac{15}{50} A = 0.3 A$$
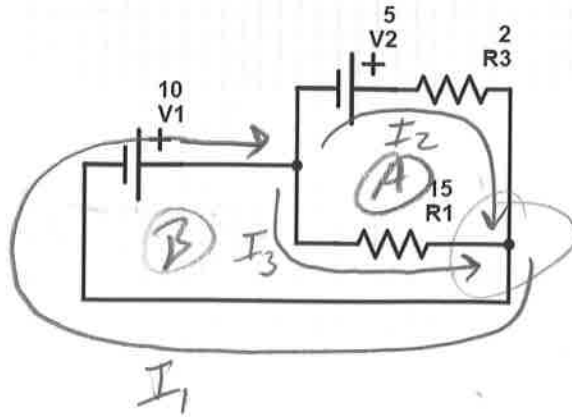
$$I_1 = \frac{27}{2} A + \frac{15}{50} A = 13.8 A$$



Junction:

$$I_1 = I_2 + I_3$$

$$10V - 15I_3 = 0$$

$$5V - 2I_2 + 15I_3 = 0$$


Loop B (cw)

Loop A (cw)

$$I_3 = \frac{10}{15} A = \frac{2}{3} A = 0.67 A$$

$$I_2 = 7.5 A$$

$$I_1 = 8.17 A$$

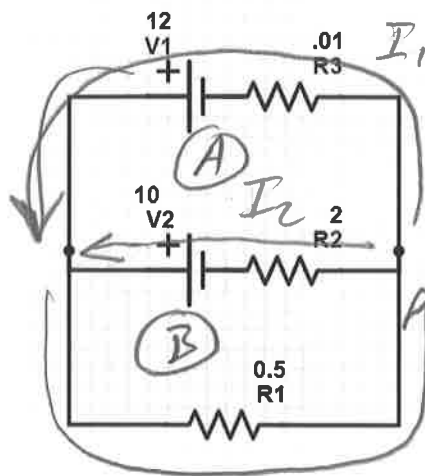

Superposition Rule

$$I_1 + I_2 = I_3$$

$$I_2 = I_3 - I_1$$

I_3

Loop A:
(ccw)

$$12V - 10V + 2I_2 - 0.01I_1 = 0$$

$$I_2 = 0.005I_1 - 1V$$

Loop B:
(ccw)

$$10V - 0.5I_3 - 2I_2 = 0$$

$$I_2 = 5V - 0.25I_3$$

$$0.005I_1 - 1V = 5V - 0.25I_3$$

$$-0.02I_1 + 24V = I_3$$

$$0.005I_1 - 1V = -0.02I_1 + 24V - I_1$$

$$1.025I_1 = 25V$$

$$I_1 = \frac{25V}{1.025 \Omega}$$

$$I_1 = 24.4A$$

$$I_2 = 0.005(24.4A) - 1V$$

$$I_2 = -0.878A$$

As drawn

$$I_3 = I_1 + I_2$$

$$I_3 = 23.5A$$

~~I_2 is drawn backward!~~
~~(Negative)~~